
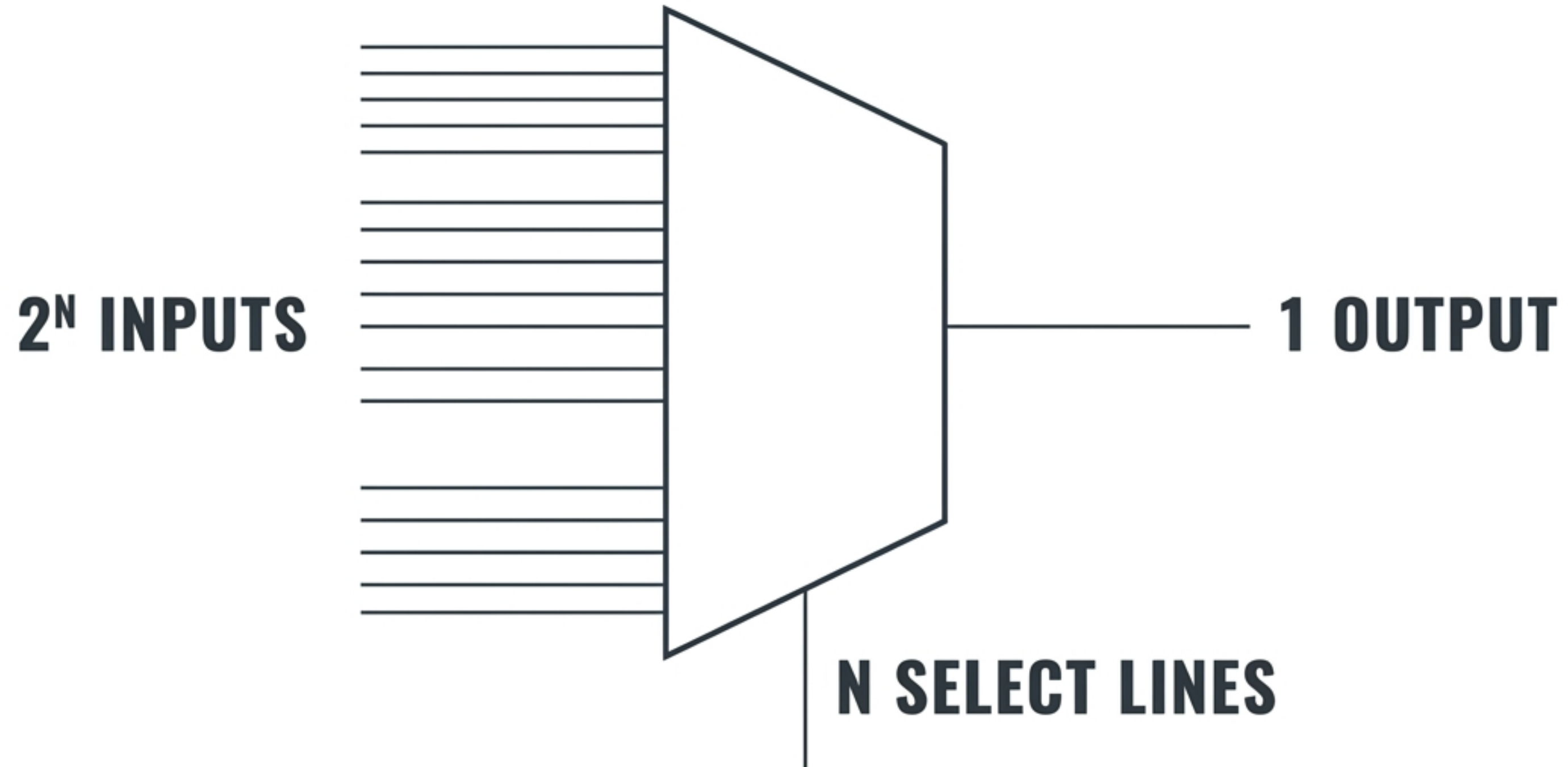


MUX : DATA SELECTOR

MANY-TO-1

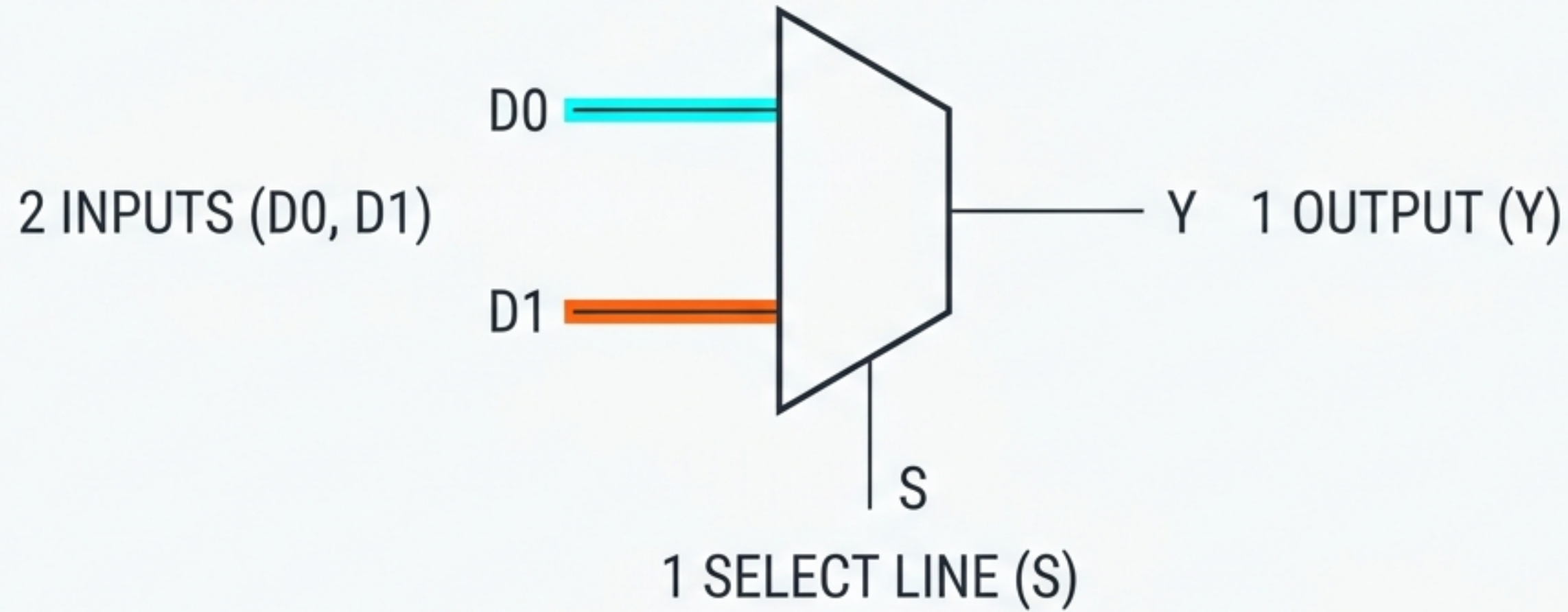


2-TO-1 MUX



$$Y = S'D0 + SD1$$

4-TO-1 MUX

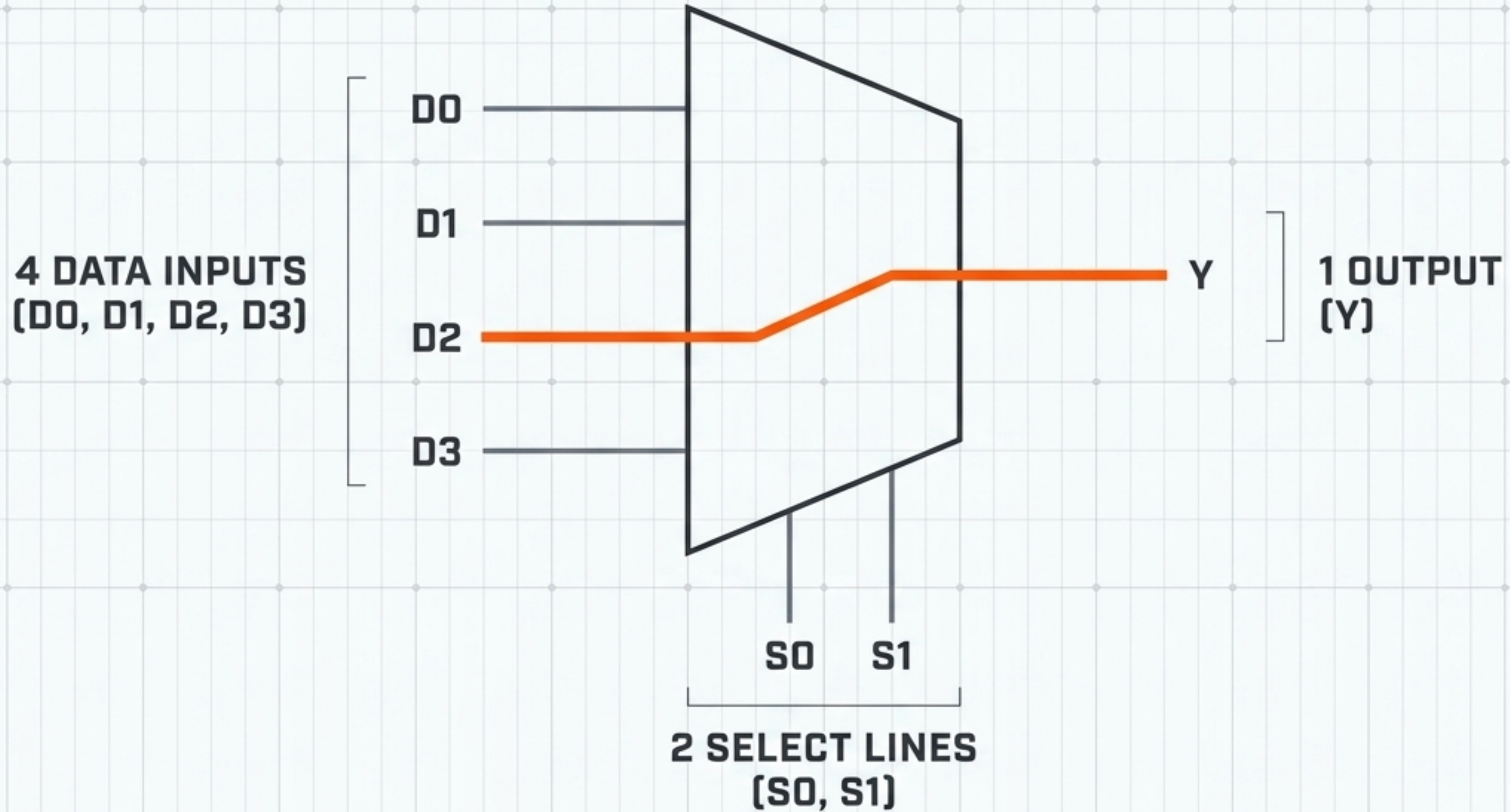

SMART TV ANALOGY

